 


# Midterm Study

Monday, November 5, 2018 12:53 PM

## (1) Elmore Delay

$$t_{pd_{0 \rightarrow i}} = \sum R_{ij} C_j$$



$$t_{pd@v1} = \sum R_{1j} C_j = R_1 C_1 + R_1 C_2$$

$$t_{pd@v2} = R_1 C_1 + (R_1 + R_2) C_2$$

Parallel  $\rightarrow R$


Series  $\rightarrow R/2$

Worst case delay = filled "buckets" capacitors at max.

$$\text{charging } (V_{dd} \rightarrow Y) = t_{pdr} = 6C * R + (2C) \left(\frac{R}{2}\right)$$


$$\text{discharg}(gnd \rightarrow Y) = t_{pdf} = \left(\frac{R}{2}\right)(2C) + R(6C)$$

$$t_{pd_{avg}} = (t_{pdr} + t_{pdf})/2$$

 

 
## (2) Logical Efforts

def... measure of input capacitance for same condition (chrg/disc)



Charging

 


Discharging

Add capacitive values with respect to proper ratio of that logic gate

$$g_c = \frac{5}{6} = \frac{g_o}{g_{dc}}$$

$$g_d = \frac{5}{3} = \frac{g_o}{g_{dd}}$$

$$g_{av} = \frac{g_c + g_d}{2} =$$

 

$$\hat{f} = (F)^{\frac{1}{N}} = \sqrt{F}$$

$N = \log_4(X) \Rightarrow$  Get N between 3 and 4 for best delay

$$\text{Fanout} = h = \frac{xC}{C_{in}}$$

## Delay

$$d = gh + p$$

$$f = \text{effort delay} = gh$$

$$g = \text{logical delay}$$

$$h = \text{electrical effort} = \frac{C_{out}}{C_{in}}$$

$$p = \text{parastic delay}$$

## Logical Effort

Gate	1	2	3	N
Inv	1	-	-	-
NAND	-	4/3	5/3	(n+2)/3
NOR	-	5/3	7/3	(2n+1)/3
Mux	2	2	2	2
XOR		4,4	6,12,6	

## Parasitic Delay

Gate	1	2	3	N
Inv	1	-	-	-
NAND	-	2	3	n
NOR	-	5/3	7/3	n
Mux	2	4	6	2n
XOR		4	6	

## (3) Power Consumption

$$P_{dyn} \cong P_{sw} + P_{short} \rightarrow 0$$

$$P_{sw} = \alpha C V_{dd}^2 f$$

$$P_{static} = V_{dd} \cdot \sum I_{leak} \Rightarrow \begin{cases} \text{gate} \rightarrow 50\% \\ \text{subthreshold} \rightarrow 50\% \\ \text{junction} \cong 0\% \end{cases}$$

- 5.1 You are synthesizing a chip composed of random logic with an average activity factor of 0.1. You are using a standard cell process with an average switching capacitance of 450 pF/mm<sup>2</sup>. Estimate the dynamic power consumption of your chip if it has an area of 70 mm<sup>2</sup> and runs at 450 MHz at  $V_{DD} = 0.9$  V.

$$\alpha = 0.1$$

$$\frac{C}{\text{mm}^2} = 450 \frac{\text{pF}}{\text{mm}^2}$$

$$A = 70 \text{ mm}^2$$

$$f = 450 \text{ MHz}$$

$$V_{DD} = 0.9 \text{ V}$$

$$P_{dym} = \alpha C V_{DD}^2 f = (0.1) * \left( \frac{450 \text{ pF}}{\text{mm}^2} * 70 \text{ mm}^2 \right) * (0.9^2) * (450,000,000) = \mathbf{1.15 \text{ W}}$$

#### Example 5.4

Consider the system-on-chip from Example 5.1. Subthreshold leakage for OFF devices is 100 nA/ $\mu\text{m}$  for low-threshold devices and 10 nA/ $\mu\text{m}$  for high-threshold devices. Gate leakage is 5 nA/ $\mu\text{m}$ . Junction leakage is negligible. Memories use low-leakage devices everywhere. Logic uses low-leakage devices in all but 5% of the paths that are most critical for performance. Estimate the static power consumption.

$$I_{low} = \frac{100 \text{ nA}}{\mu\text{m}}$$

$$I_{high} = \frac{10 \text{ nA}}{\mu\text{m}}$$

$$I_{gate} = \frac{5 \text{ nA}}{\mu\text{m}}$$

$$\lambda = 65 \text{ nm process}$$

$$\text{Logic width} = 12 \lambda$$

$$\text{Memory width} = 4 \lambda$$

$$\text{Logic uses low in all but 5\%}$$

$$\text{Channel Lengths drawn} = .025 \mu\text{m}$$

$$\#_{logic} = 50 \cdot 10^6$$

$$\#_{mem} = 950 \cdot 10^6$$

$$T_{highlog_{5\%}} = 50 \cdot 10^6 (0.05)(12\lambda) \left( \frac{0.025 \mu\text{m}}{\lambda} \right) = 0.75 \cdot 10^6 \mu\text{m}$$

$$T_{lowlog_{95\%}} = 50 \cdot 10^6 (0.95)(12\lambda) + 950 \cdot 10^6 (4\lambda) \left( \frac{0.025 \mu\text{m}}{\lambda} \right) = 109.25 \cdot 10^6 \mu\text{m}$$

$$I_{logsub} = 0.75 \cdot 10^6 (100 \text{ nA}) + 109.25 \cdot 10^6 (10 \text{ nA}) / 2 = 584 \text{ mA}$$

$$I_{gate} = 0.75 \cdot 10^6 \mu\text{m} * \frac{100 \text{ nA}}{\mu\text{m}} \left( \frac{\left( 5 \frac{\text{nA}}{\mu\text{m}} \right)}{2} \right) = 275 \text{ mA}$$

$$P_{static} = 275 + 584 = \mathbf{859 \text{ mA}}$$

- 5.10 Design a header switch for a power gating circuit in a 65 nm process. Suppose the pMOS transistor has an ON resistance of about 2.5 k $\Omega \cdot \mu\text{m}$ . The block being gated has an ON current of 100 mA. How wide must the header transistor be to cause less than a 2% increase in delay?

$$\lambda = 65 \text{ nm process}$$

$$R_{on} = 2.5 \text{ k}\Omega \cdot \mu\text{m}$$

$$R = \frac{2.5}{0.065} = 38.46 \text{ k}\Omega$$

$$I_{on} = 100 \text{ mA}$$

$$\text{Delay increase} = 0.02 = 2\%$$

$$R_{eff} = \frac{20 \text{ mV}}{100 \text{ mA}} = 0.2 \Omega$$

$$W = 2.5 \text{ k}\Omega \cdot \mu\text{m} / 0.0002 \text{ k}\Omega = 12,500 \mu\text{m} = \mathbf{12.5 \text{ mm}}$$